
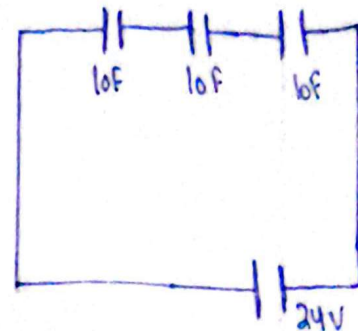



Nama : Muhamad Ripaldi

Kelas : 1IA04

NPM : 50425688

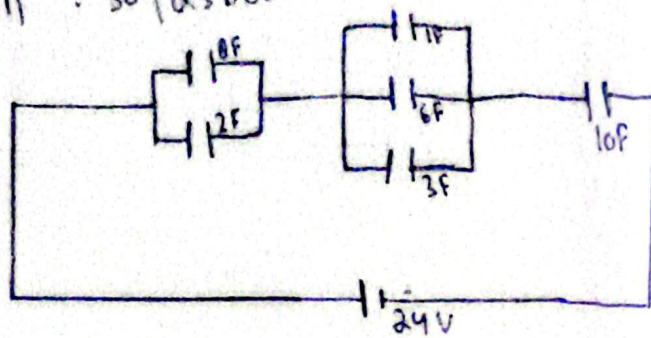

$$C_{gab} = 3,33F$$

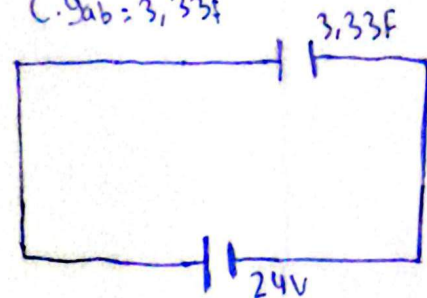

Hitung:

$$\begin{aligned} a). C_{gab} &= \frac{1}{C_{gab}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \\ &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{10} + \frac{1}{6} + \frac{1}{10} \rightarrow \\ \frac{1}{C} &= \frac{3}{6} \quad \frac{1}{1} = \frac{10}{3} = 3,33 F // \end{aligned}$$

$$\begin{aligned} b). V_{8F} &= Q_{tot} = C_{gab} \cdot V_0 \\ &= \frac{10}{3} \cdot 24 = 80C \end{aligned}$$

$$V_{8F} = V_{2F} = \frac{Q_{tot}}{C_{8F}} = \frac{80}{10} = 8V //$$

$$\begin{aligned} c). Q_{2F} &= Q = C \cdot V \\ Q_{2F} &= 2F \cdot 8V \\ &= 2F \cdot 8V = 16C // \end{aligned}$$

$$d). V_{6F} : V_{8F} = 8V$$

$$\begin{aligned} e). Q_{3F} &= Q = C \cdot V \\ Q_{3F} &= 3F \cdot V_{3F} = 3F \cdot 8V = 24C // \end{aligned}$$

$$\begin{aligned} f). W_{10F} &= \frac{1}{2} \cdot C_{10F} \cdot (V_{10F})^2 \\ &= \frac{1}{2} \cdot 10F \cdot 8^2 \\ &= \frac{1}{2} \cdot 10F \cdot 64 = 320 \text{ Joule} // \end{aligned}$$